

ECE337 hw-1


Name: Ti-Wei Chen mg account: mg35 Date: 09/11/2020 Collaborator: None

 Top Level Diagram for Timing Recover Circuit




Sync Edge Detector

 

 

When count = 6 bits period, stop = 1. There's no next count, the count updates on inputs clock period.

60 -> 12 Clock Divider

 

60MHz to 12 MHz. Count to 5 every clock cycle while the flag == 1, then generate pulse when count == 0.