

Design Exercise

RTL Block Diagrams for a timing recovery circuit

- 10 pts
- Create your own design (but can discuss with teams)
- Write short description for each block, state transition diagrams for any state machines, indicate number of Flip-flops in each block
- Include your name, lab section, mg account, and date at top
- Collaboration with one or two other people is permitted, but each person is expected to prepare their own solution.
- If you collaborated, give your collaborator's name and briefly describe how you collaborated. Or state that you worked alone.
- The solution should either be prepared electronically or very nearly drawn and scanned and then uploaded in Brightspace

1

Updated 9/1/2020

1

Concept

- Some serial interfaces rely on the receiving interface to produce a sequence of timing pulses that are synchronized to the incoming data.
- The sequence of pulses will not stay synchronized to the incoming data unless your design continually adjusts to the incoming data bits.
- Your task: draw a hierarchical RTL block diagram for a circuit which produced a sequence of pulses, one per incoming data bit.

2

Updated 9/1/2020

2

Design Exercise Specs

Clock/Reset	Inputs	Outputs
60 MHz clock called Clk , (All flip-flops must run on this clock)	D_i : (async.) Serial data input. Input should be 1 when no data is transmitted	Shift_en_o : a timing pulse that is asserted each time a new data bit is received
Asynchronous active low reset, nRst Input of zero forces count to 0.		Timing pulses should cease if D_i does not change for more than 6 consecutive bit periods

Asynchronous inputs must be passed through a synchronizer.

3

Updated 9/1/2020

3


Design Exercise Specs

Top Level Block per...	Diagram for each top level block	Other Requirements
Counter	Registers	Indicate number of bits on all busses
State Machine	Next state logic	compute number of flip-flops required
Other major functional blocks	Output logic	Synchronizers for all asynchronous inputs including reset
	Other combinational functions	

4

d 9/1/2020

4

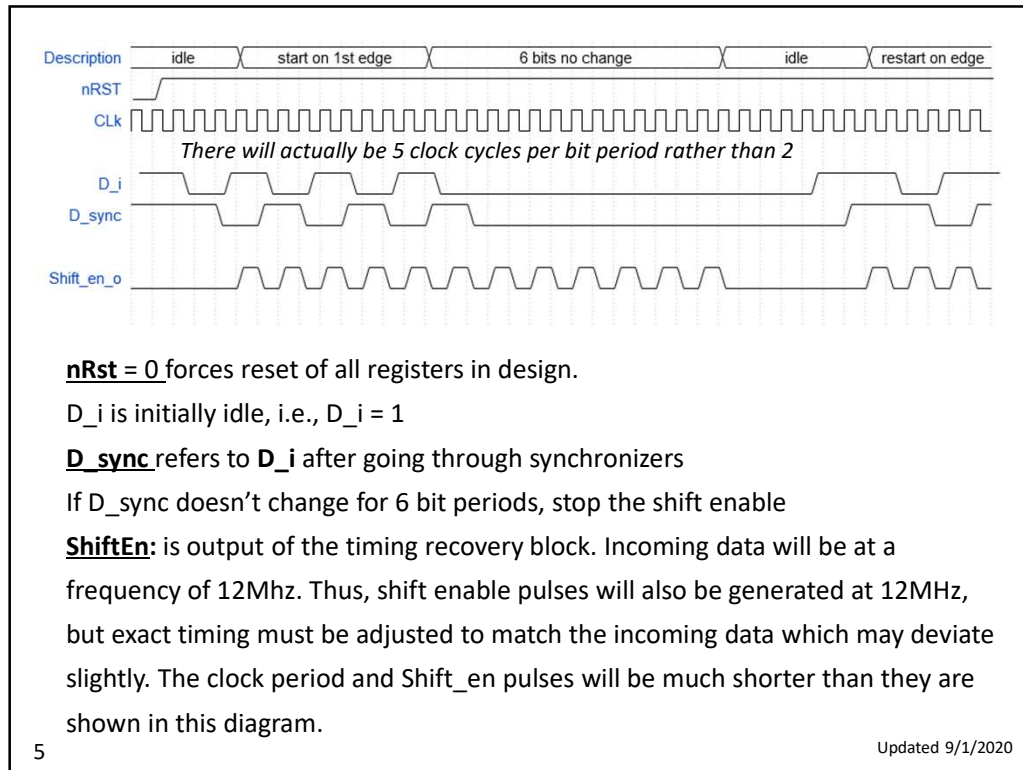

5

Tips

- Draw a **functional block diagram 1st** and make sure that it accounts for the required functions and interface signals. Then add clock and reset signals were necessary. This will become the top diagram in your hierarchical RTL block diagram.
- For each block, you will need to prepare a supporting diagram (see sample solution to prior RTL homework)
- A sample of a prior assignment will be posted in BrS to give you an idea of the expected format.

6

Updated 9/1/2020

6

Tips

- Your design should include:
 - A synchronous edge detector (to detect rising and falling edges on D_i). Resembles a synchronizer + a gate to compare the FF outputs.
 - A clock divider that produces pulses at 12MHz. Every transition on D_i should cause the clock divider to restart.
- Make sure that the shift enable pulses stop if 6 clock divider pulses occur consecutively without a change in D_i

7

Updated 9/1/2020

7

Tips

- Include a synchronizer on the input D_i
- You are expected to partition the design into small enough functional blocks so that each block would be relatively simple to design and debug.
- If you come to the Tuesday morning lecture review or office hours, we can discuss some of the blocks you will need and how to get started preparing the solution.

8

Updated 9/1/2020

8